

EEM412 Course
Introduction to IC Design – II

Instructor
Dr. İsmail Enis Ungan

Subsystem Design

- Digital functions may be divided into the categories of;
 - data-path operators
 - memory elements
 - control structures
 - I/O cells
- Data-path Operators
 - Data is usually wide
 - Function can be implemented by n identical circuits (bit-slice).
 - Operators may be sequenced in time or in space, therefore they are placed next to each other.
 - Generally data flow is in one direction, while control signals are orthogonal to data flow.

Data-Path Operators

- Data-path Operators
 - Addition/Subtraction
 - Parity Generators
 - Comparators
 - Zero/One Detectors
 - Binary Counters
 - Boolean Operations - ALUs
 - Multipliers
 - Shifters

Addition/Subtraction

- Full Adder

$$SUM = ABC + AB'C' + A'B'C + A'BC'$$

$$SUM = C(AB + A'B') + C'(AB' + A'B)$$

$$SUM = A \oplus B \oplus C$$


$$CARRY = AB + AC + BC$$

$$CARRY = AB + C(A + B)$$

$$\Rightarrow SUM = ABC + (A+B+C) CARRY'$$


- n-bit Ripple Carry Adder

 - Built from one-bit full adders.
- Adder becomes subtractor by inverting one of the two inputs and providing '1' as the carry input.




Addition/Subtraction

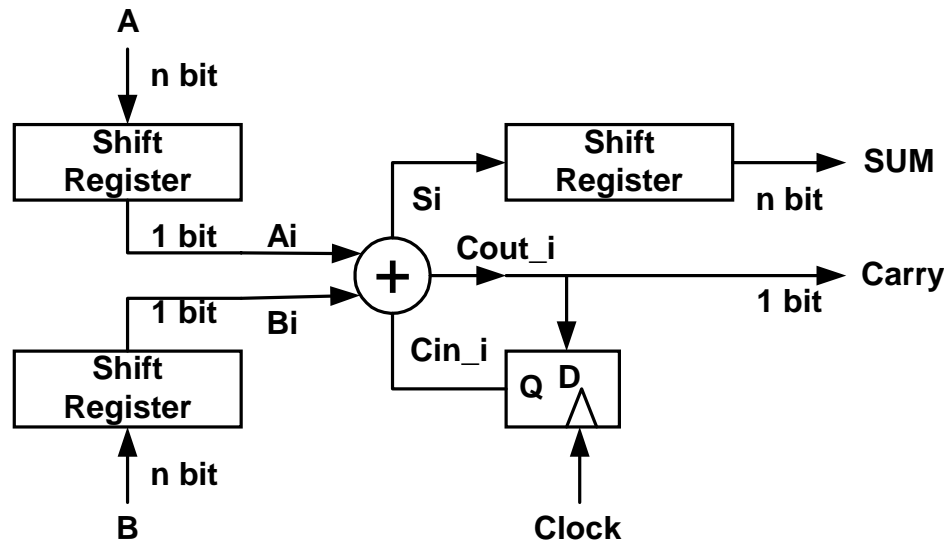- Serial Adder
 - Requires a number of very short clock cycles to add two n-bit numbers.
 - Can be implemented on nybbles (4-bit words).
 - If both SUM and CARRY are registered at each cycle then adder is called carry-save adder. Hence, Serial Adder is a carry-save adder.




Addition/Subtraction

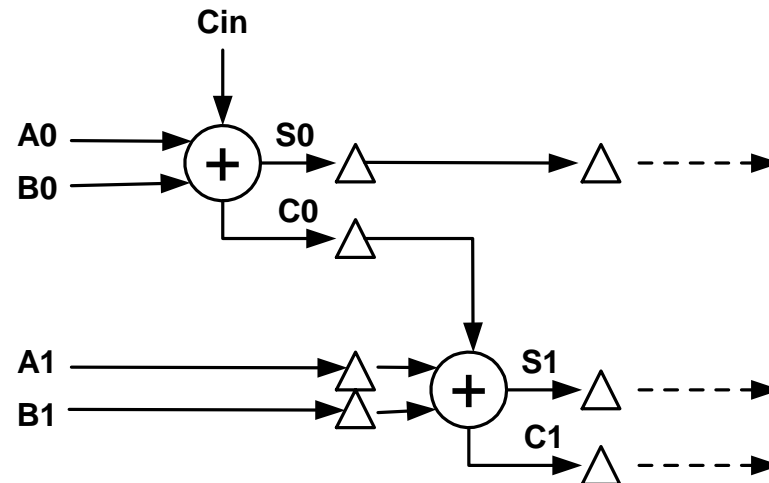- Pipelining
 - Example: Both sum and carry are saved at the full-adder outputs. Delay elements are simply D-FFs.



Addition/Subtraction

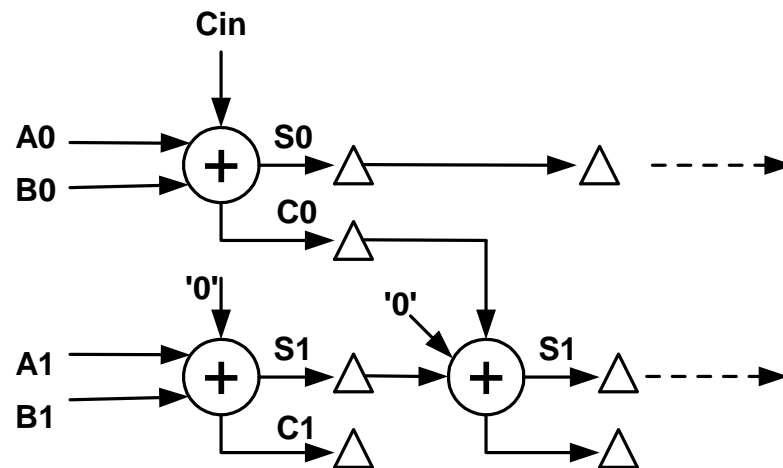- Pipelining
 - Example: That can be extended to add 4 numbers.





Addition/Subtraction

- Transmission-Gate Adder

- Less MOSFETs.

$$SUM = A \oplus B \oplus C = \begin{cases} C & \text{when } A \oplus B = 0 \\ \overline{C} & \text{when } A \oplus B = 1 \end{cases}$$
  
$$CARRY = \begin{cases} C & \text{when } A \oplus B = 1 \\ A & \text{when } A \oplus B = 0 \end{cases}$$



Addition/Subtraction

- Carry-Look-Ahead Adder

$$C_0 = A_0 \cdot B_0 + (A_0 + B_0) \cdot C_{in}$$

$$C_1 = A_1 \cdot B_1 + (A_1 + B_1) \cdot C_0$$

↓

$$C_i = A_i \cdot B_i + (A_i + B_i) \cdot C_{i-1}$$


$$C_i = G_i + P_i \cdot C_{i-1}$$

⇓

$$C_i = G_i + P_i \cdot G_{i-1} + P_{i-1} P_i \cdot G_{i-2} + \dots + P_i \dots P_0 \cdot C_{in}$$

$$S_i = A_i \oplus B_i \oplus C_{i-1}$$

 
$$S_i = P_i \oplus C_{i-1} \quad \text{if} \quad P_i = A_i \oplus B_i$$



Addition/Subtraction

- Carry Generator by Dynamic Logic

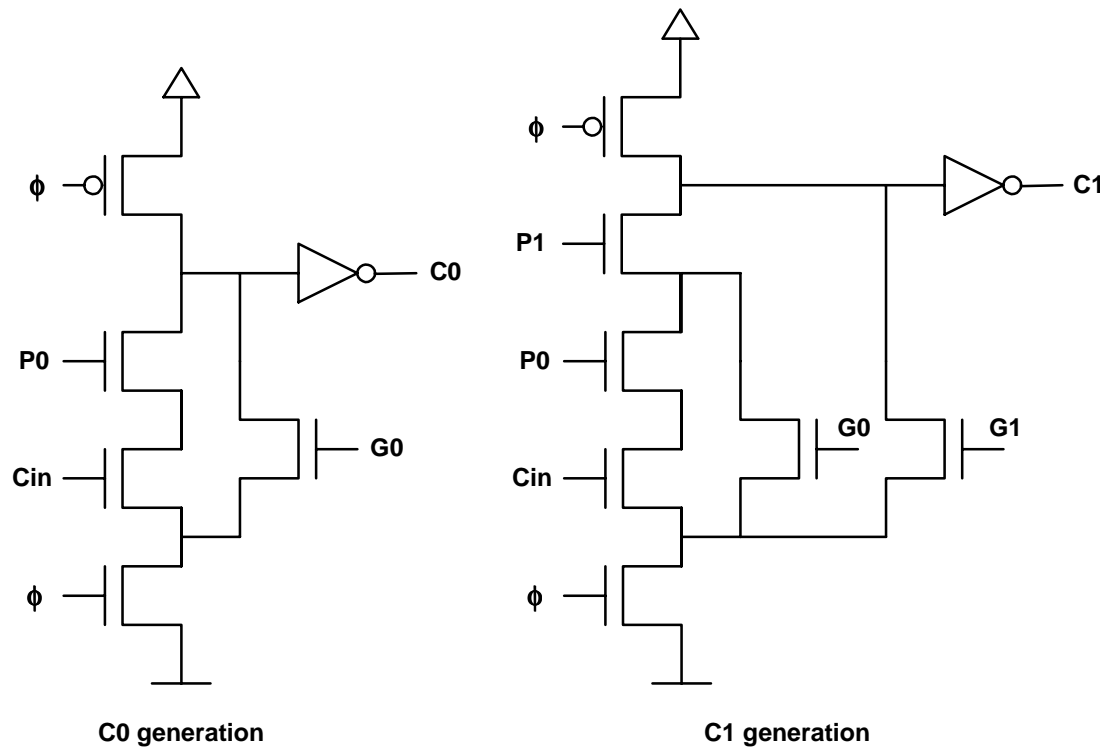
$$C_i = G_i + P_i \cdot G_{i-1} + P_{i-1}P_i \cdot G_{i-2} + \dots + P_i \dots P_0 \cdot C_{in}$$



Addition/Subtraction


- Manchester Carry Chain

$$C_i = G_i + P_i \cdot C_{i-1}$$

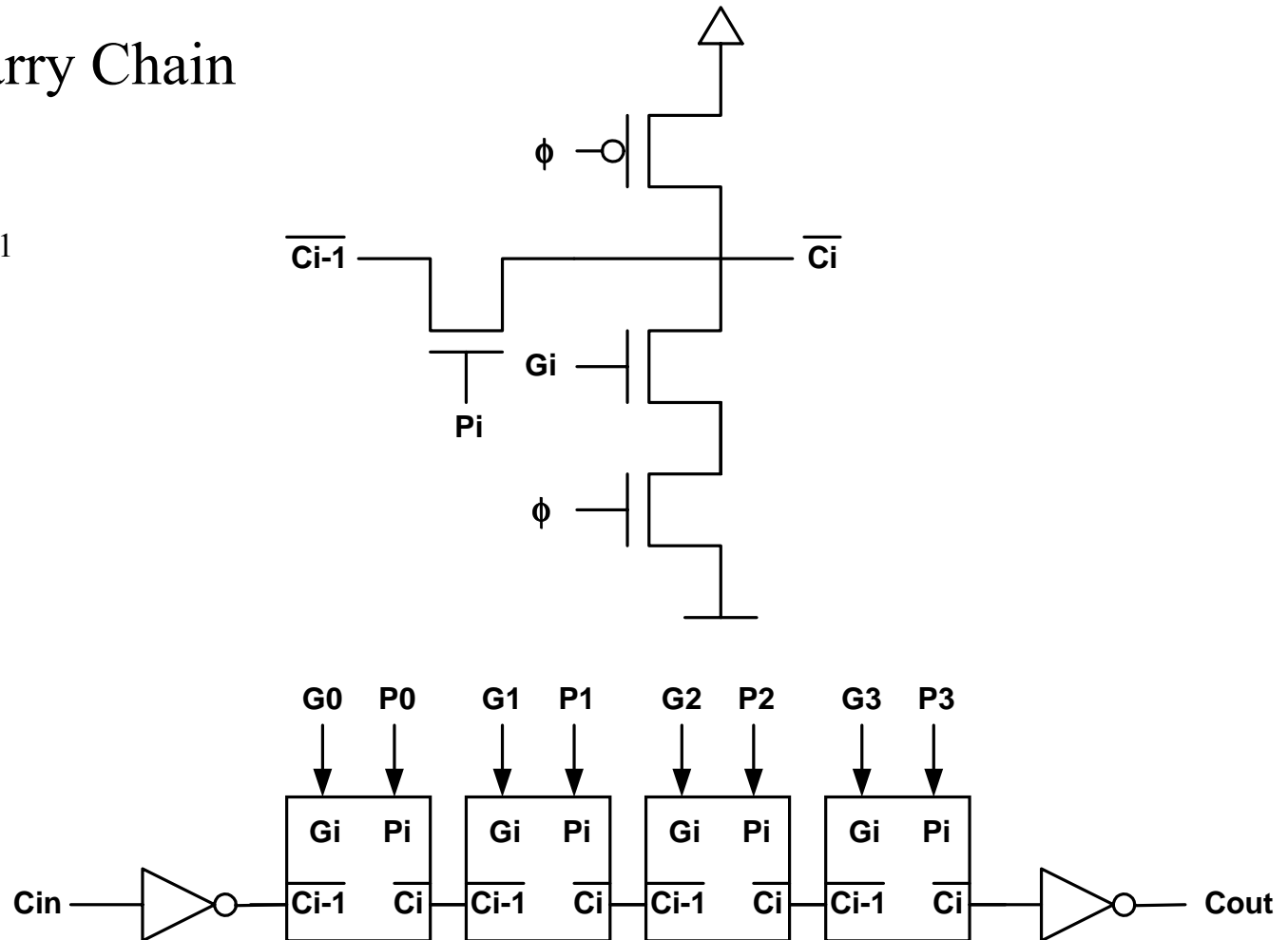


Addition/Subtraction

- Carry Select Adder

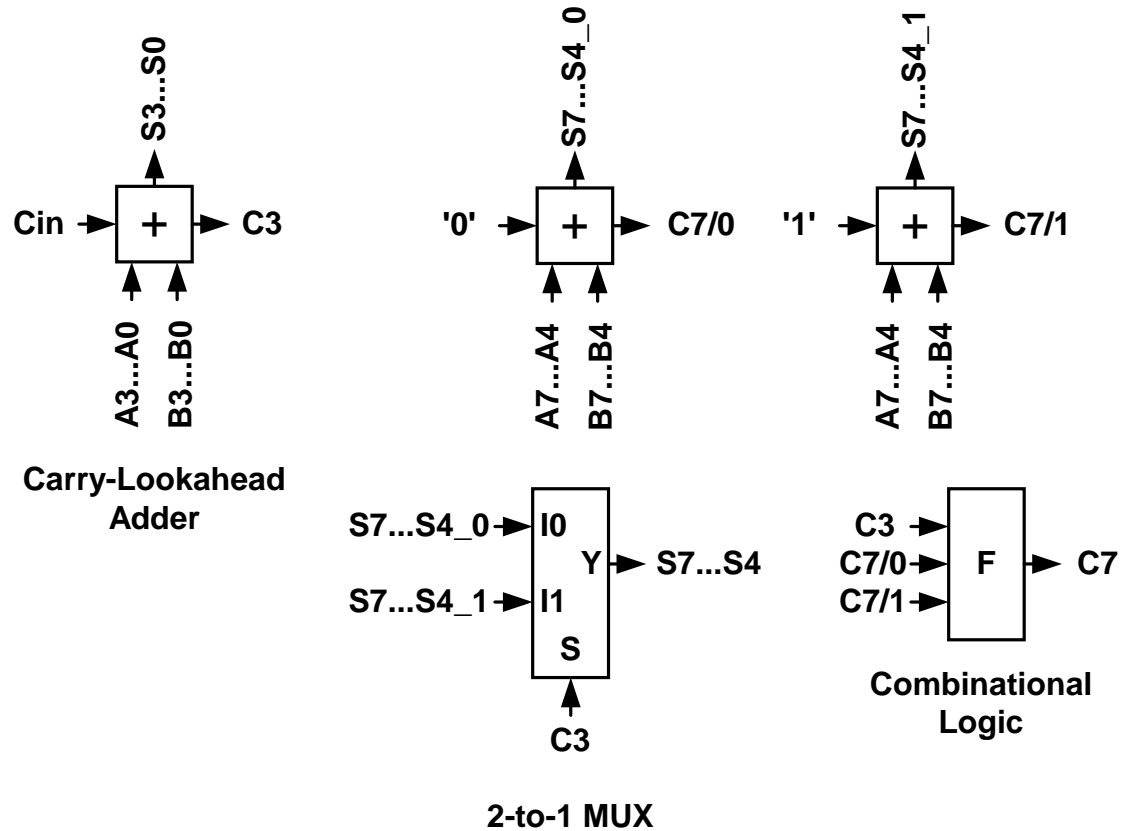

Addition/Subtraction

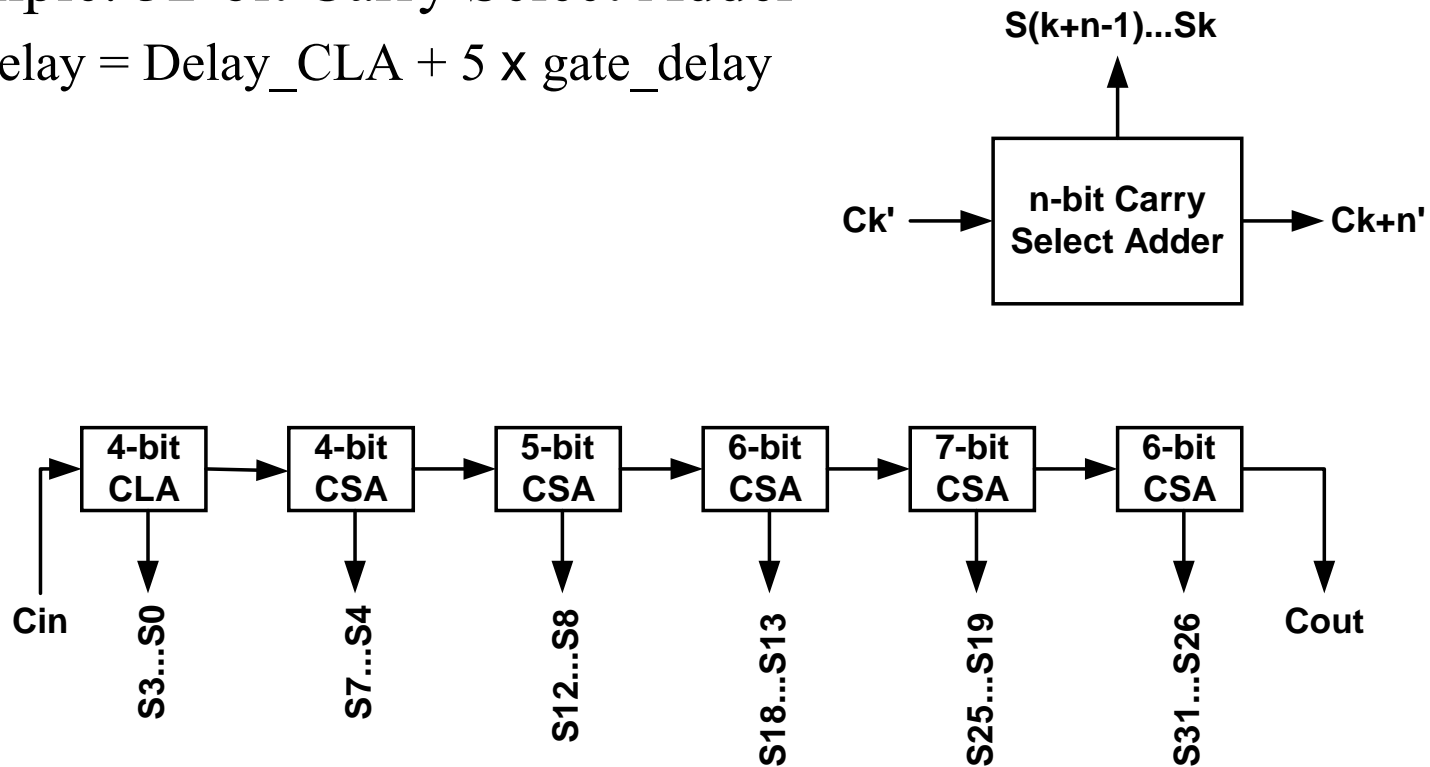- Example: 32-bit Carry Select Adder
 - Delay = Delay_CLA + 5 x gate_delay



Addition/Subtraction


- Conditional Sum Adder

$$SUM = \begin{cases} A \oplus B & \text{when } C_{in} = 0 \\ \overline{A \oplus B} & \text{when } C_{in} = 1 \end{cases}$$

$$CARRY = \begin{cases} A \cdot B & \text{when } C_{in} = 0 \\ A + B & \text{when } C_{in} = 1 \end{cases}$$

- Very Wide Adders

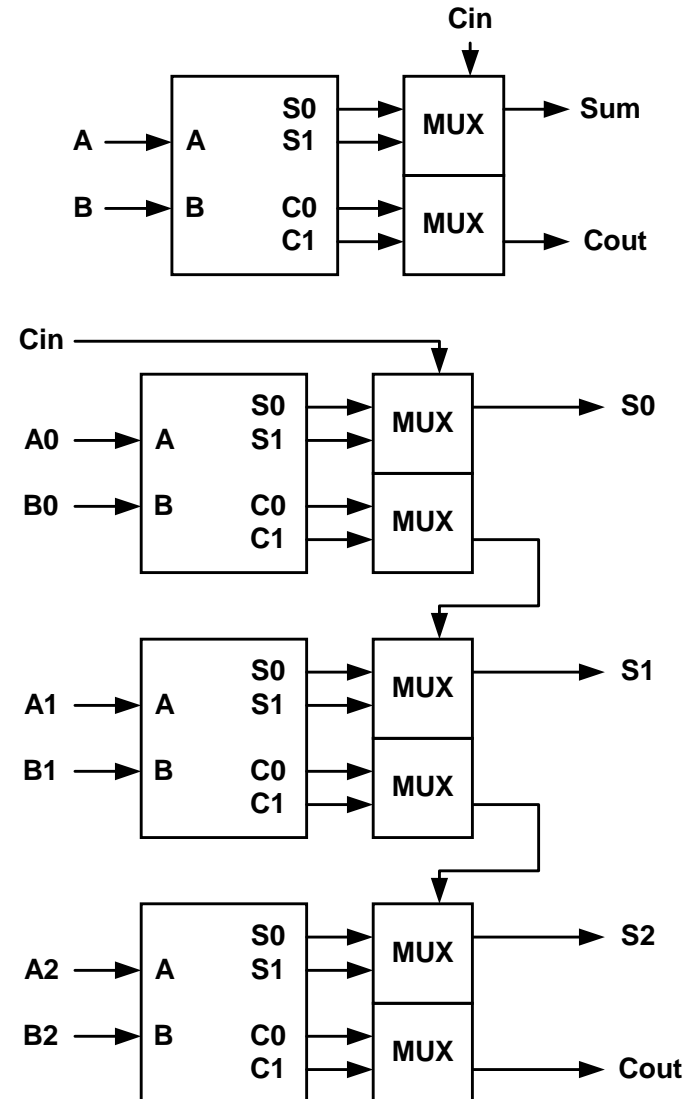- Adders with word width greater than 32 bits can be constructed by applying hierarchy and modularity by combining adders with smaller widths.



Data-Path Operators


- Parity Generators
 - Detects whether the number of ones in an input word is even or odd.

$$PARITY = A_0 \oplus A_1 \oplus A_2 \oplus \dots \oplus A_n$$


- Comparators
 - Compares the magnitude of two binary numbers.
- Zero/One Detectors
 - Detects all ones/zeros on a word.

Data-Path Operators

 - Binary Counters
 - Asynchronous counters
 - Synchronous counters



Asynchronous

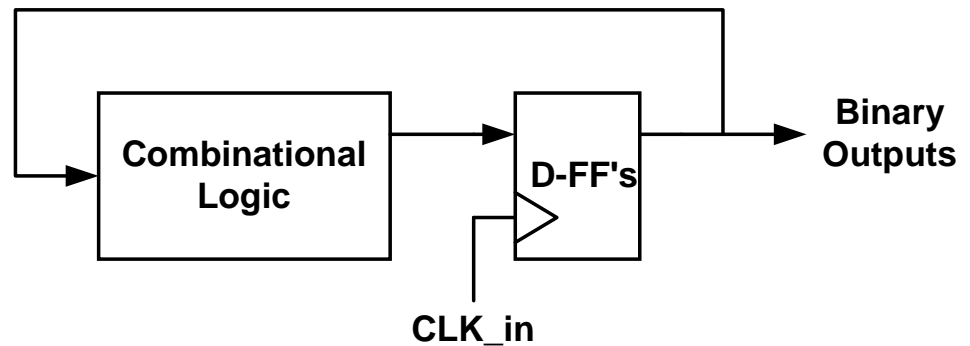

Synchronous

Data-Path Operators

- Boolean Operations - ALUs
 - Arithmetic (addition/subtraction) and Boolean operations are performed.
 - Any Boolean function can be implemented by using TGs and MUXes.
- Multiplication
 - X is m-bit unsigned binary number
 - Y is n-bit unsigned binary number


$$X = \sum_{i=0}^{m-1} x_i 2^i$$

$$Y = \sum_{j=0}^{n-1} y_j 2^j$$

$$P = X \times Y = \sum_{i=0}^{m-1} \sum_{j=0}^{n-1} x_i y_j 2^{i+j}$$

Data-Path Operators

- Array Multiplication

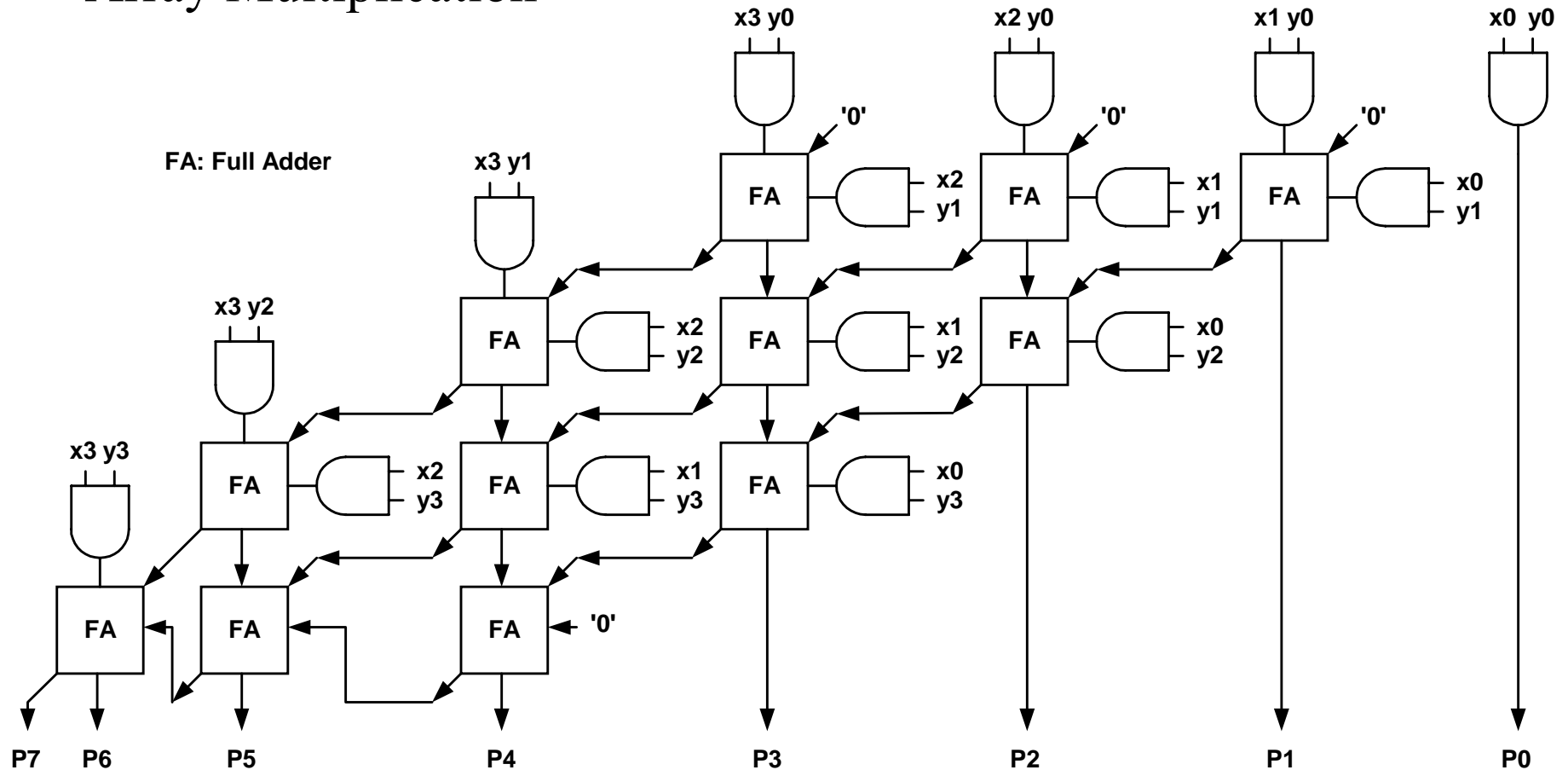


Multiplication

- Radix-n Multiplication
 - Aim is to reduce adders and delay.
 - Booth-recorded multiplier is a Radix-4 multiplication scheme.
- Wallace Tree Multiplication
 - Adder is a one's counter circuit.
 - 1-bit adder provides 3:2 compression in the number of bits.
 - The addition of partial products in a column of an array multiplier is actually a counting of number of ones with carry.
 - An adder that provides 5:3 compression is often used.

Multiplication

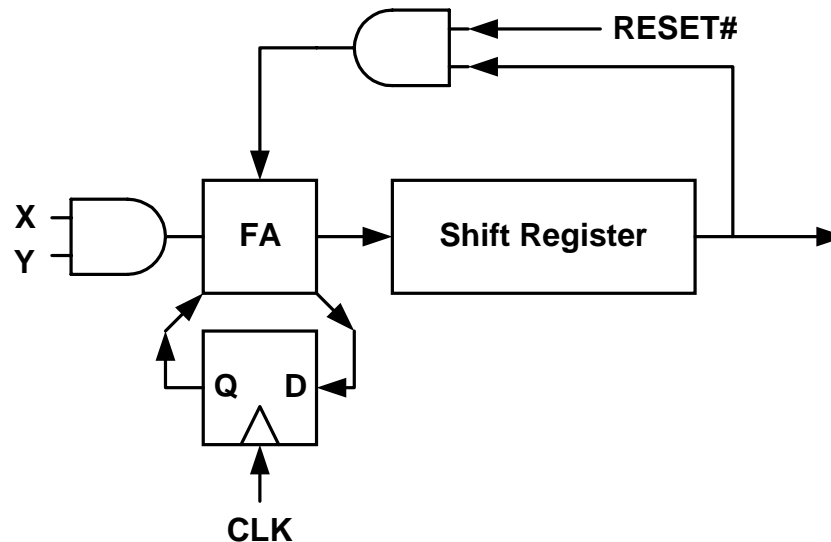- Serial Multiplication
 - X and Y are input serially at different rates.
 - Partial products are accumulated and stored in the shift register
 - Reset input is used to reset the partial sum at the beginning of multiplication cycle.
 - Product of $m+n$ bits are obtained in $m \times n$ cycles.




Data-Path Operators

- Serial/Parallel Multiplication
 - Product of $m+n$ bits are obtained in $m+n$ cycles.
- Shifters
 - Arithmetic shifting
 - Logical shifting
 - Rotation functions
 - Shuffles
 - Bit reversals/interchanges


Memory Elements

 - Random Access Memory
 - Access time is independent of the physical location of the data.
 - Memory architecture:



Memory Elements

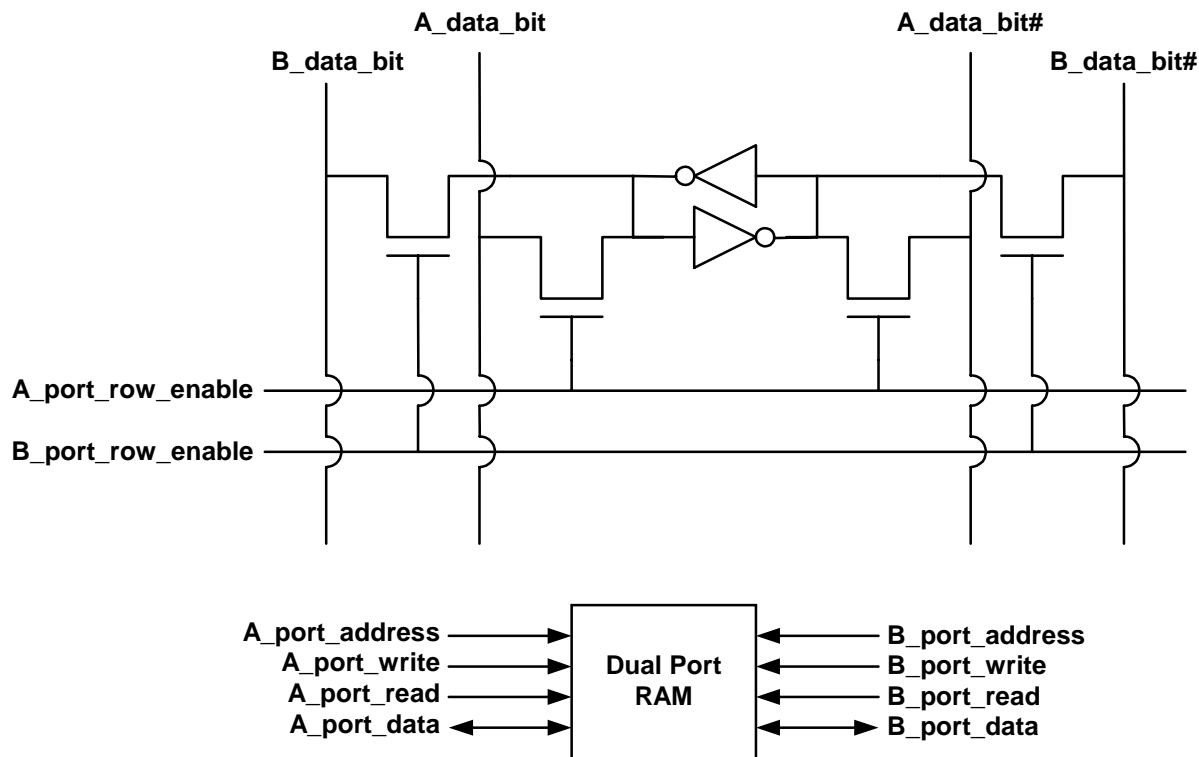- Register Files
 - Fast RAMs with multiple read and write ports
 - Example: Dual port RAM memory cell circuitry



Memory Elements

- First-In-First-Out (FIFO) Memory
 - Useful in buffering data between two asynchronous data streams.
 - FIFO memory I/O:




- Last-In-First-Out (LIFO) Memory
 - Used in sub-routine calls in uP (Stack).
- Serial-In-Parallel-Out (SIPO) Memory
 - Used to convert serial data to parallel form.



Memory Elements

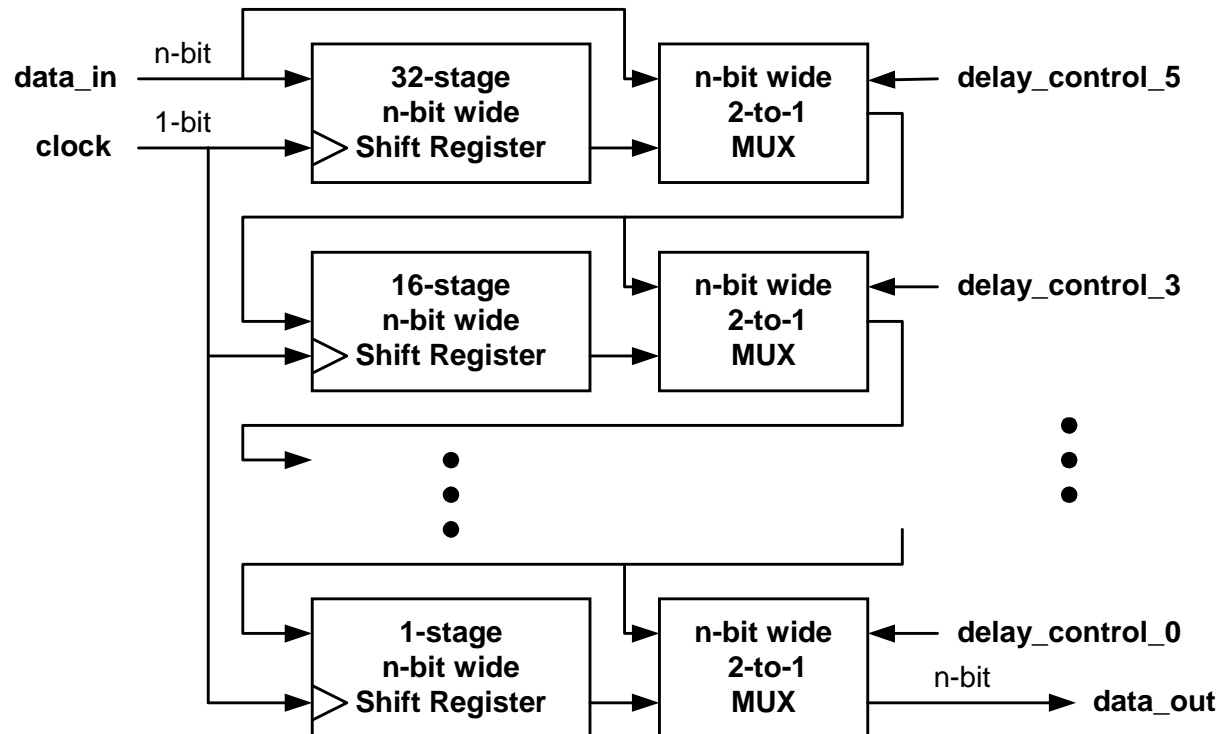- Serial-Access Memory
 - Used in signal processing for storage and delaying signals.
 - Example: Tapped delay line RTL description:





Memory Elements

- Read-Only Memory
 - Single MOSFET per bit of storage.
 - Static memory structure.
 - Bit storage even without power supply.
 - Usually implemented as a NOR array. NAND array is slow but less area.
- Content Addressable Memory
 - Compares a data word with the stored data words.
 - If one or more internal data match with the input data then internal data addresses are output as match outputs.

Memory Elements

 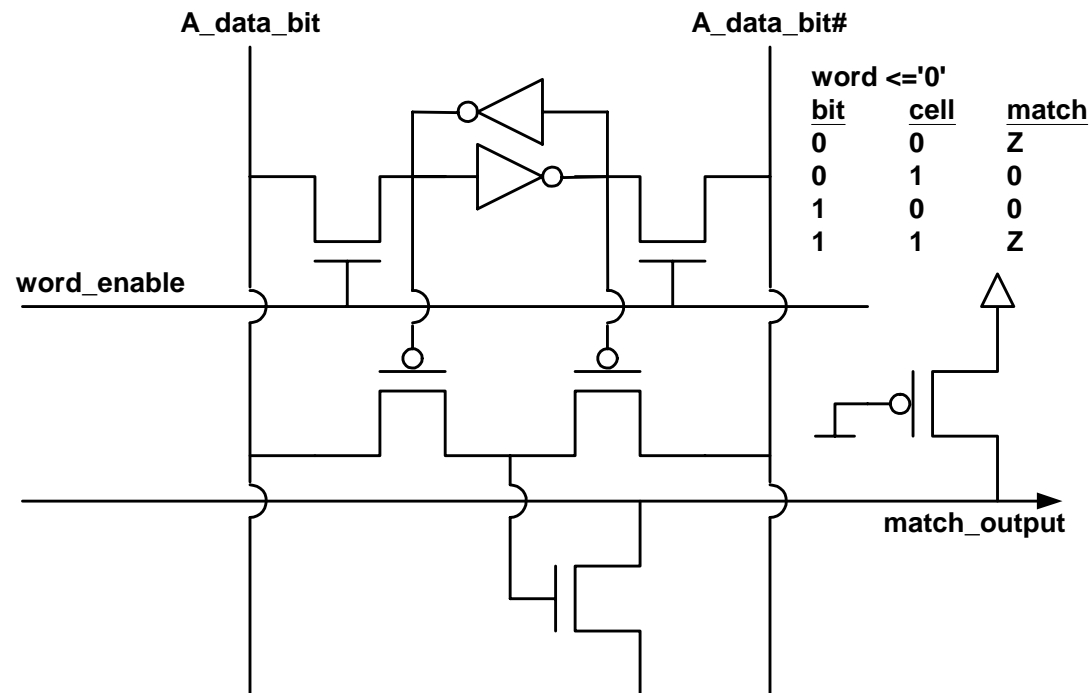
- ... Content Addressable Memory
 - CAM cell:



Control Structures

- Finite-State Machines

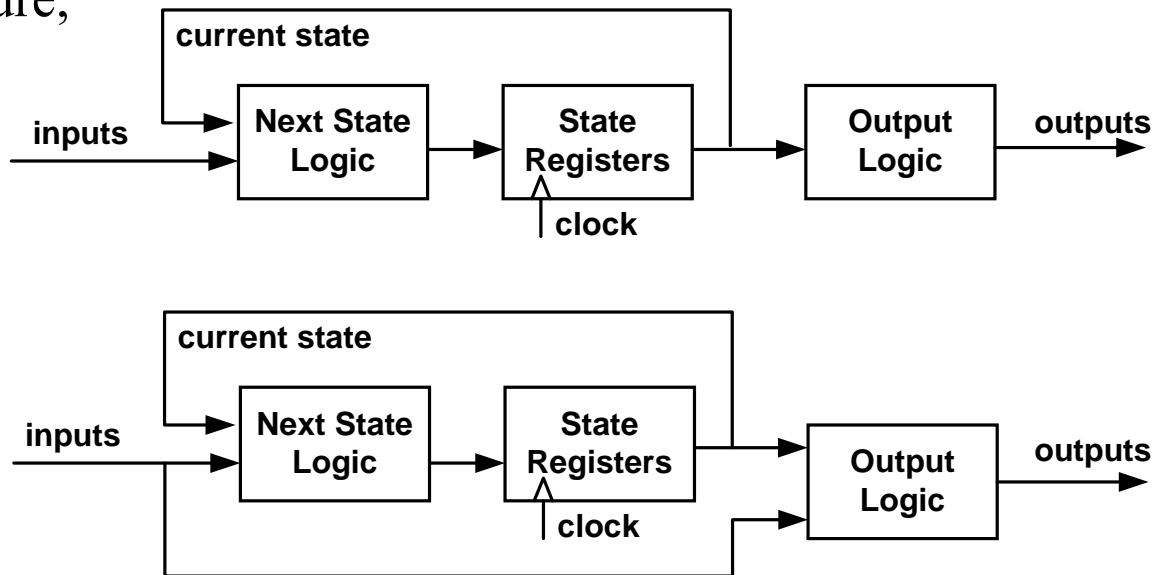- Organized structure for control sequencing/operation
- Two basic types of state machines can be designed; Mealy, and Moore.
- In Moore FSM structure, outputs are functions of state only.
- In Mealy FSM structure, outputs are functions of both state and inputs.
- Structure;



Control Structures

- FSM Design Procedure
 - Draw state-transition diagram
 - Check the diagram
 - Write state equations
 - Assign binary numbers to the states
 - Construct the resulting logic and registers.
- Control Logic Implementation
 - Two-level sum-of-products logic
 - Programmable Logic Array (PLA) is a regular structure to implement combinational and sequential logic functions.
 - Typical PLA uses two-level sum-of-products AND-OR structure.

Control Structures

- ... Control Logic Implementation
 - Multi-Level logic
 - Common method for CMOS.
 - Regular gates are cascaded.
 - Many CAD tools minimize the logic for a set of Boolean functions.
 - FSMs can be directly synthesized from a high-level description.